

# PSEC5 Layout

Dec 2023

# Single Channel Overview



# Signal Transmission

32x35fF capacitor load per fast bank buffer when the corresponding fast bank is running

8x35fF capacitor load within the entire slow buffer at any given time

Discriminator + 2+10bit counter


~180u

~550u

~45u


~110u

 Layer: M6. Trace width: 2u  
Rs: 0.14 Ohm/Sq  
C: 2e-2 fF per 1u trace length



# Trigger Scheme

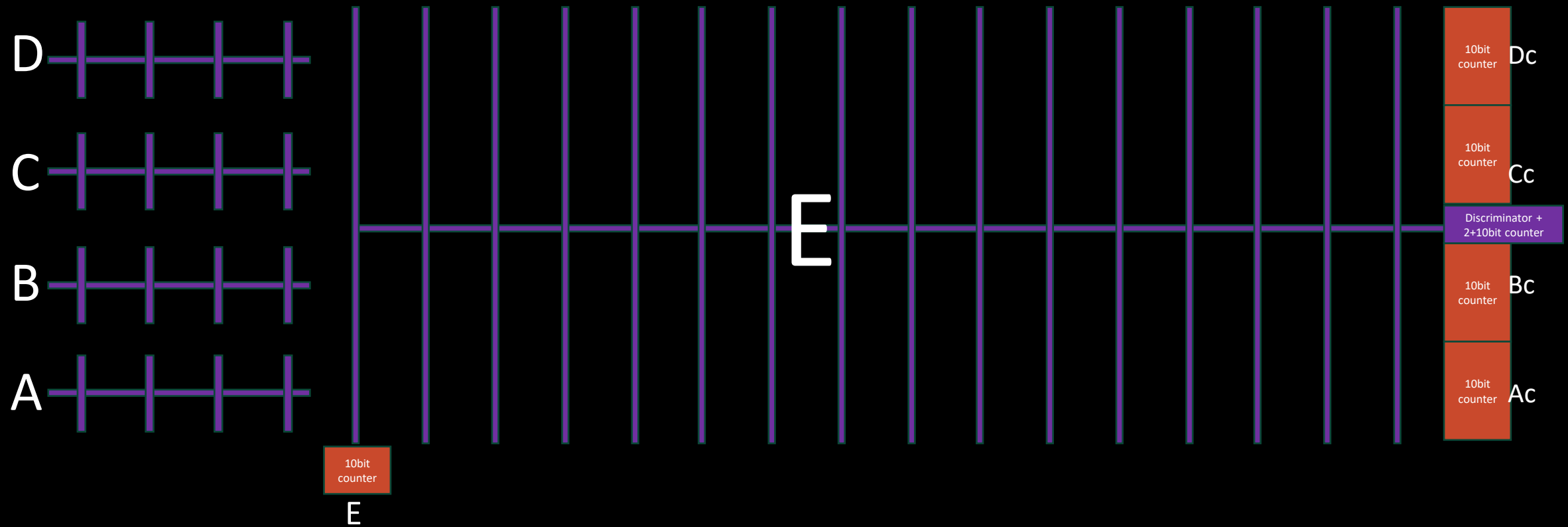0: sampling and counting. 1: holding and not counting.



# States and Trigger Scheme


States	A	Ac	B	Bc	C	Cc	D	Dc	E
stopped	1	1	1	1	1	1	1	1	1
samplingA	0	0	1	0	1	0	1	0	0
samplingB	1	1	0	0	1	0	1	0	0
samplingC	1	1	1	1	0	0	1	0	0
samplingD	1	1	1	1	1	1	0	0	0
samplingE	1	1	1	1	1	1	1	1	0
samplingA+B	0	0	0	0	1	0	1	0	0
samplingC+D	1	1	1	1	0	0	0	0	0
samplingA+B+C+D	0	0	0	0	0	0	0	0	0

Transitions	Conditions
stopped → samplingA	Start command from FPGA
samplingA → samplingB	Discri. Fired for the 1st time
samplingB → samplingC	Discri. Fired for the 2nd time
samplingC → samplingD	Discri. Fired for the 3rd time
samplingD → samplingE	Discri. Fired for the 4th time
samplingB,C,D,E → stopped	Stop command from FPGA

After roughly 800 5GHz clock cycles or 180ns since the discriminator fired for the 1<sup>st</sup> time, notify the FPGA so that it can issue the stop command

 
# Readout Scheme

There is a voltage follower at each column, 20 in total.




Each thick blue line represents 64 flip-flops running at 50MHz.  
Only one flip-flop is high at any given time.

# Clock distribution

 

10GHz CLK does not have a secondary driver in the current design!

25ps ~ 7500u  
6ps ~ 1800u

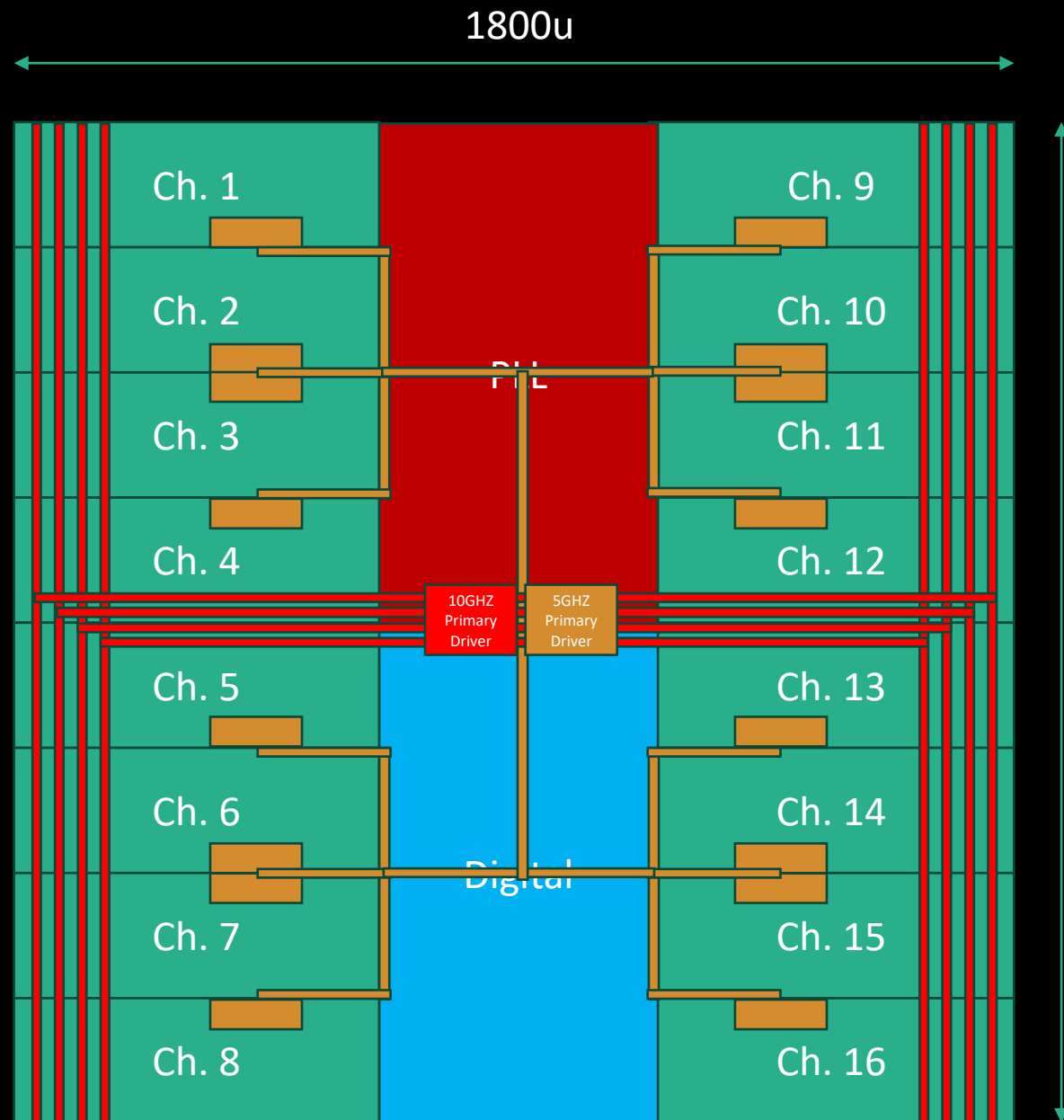

Layer: M9. Trace width: 2u  
Rs: 0.04 Ohm/Sq  
C: 2e-2 fF per 1u trace length

Layer: M9. Trace width: 2u  
Rs: 0.04 Ohm/Sq  
C: 2e-2 fF per 1u trace length



# Chip Overview(88 pins)

