

Fast Timing Electronics

Fast Timing Workshop

DAPNIA Saclay, March 8-9th 2007



Jean-François Genat **LPNHE Paris**

Outline

- Fast detectors, fast signals
- Time pick-off
- Time to Digital conversion
- State of the art
- Technologies
- Conclusion

Fast detectors, fast signals

Detector Signals:

Moving charges (in an electric field):

$$i(t) = n(t) q v(t)$$

Rise-time $i'(t) = q [n(t) v'(t) + n'(t) v(t)]$


Maximize

n electron multiplication PMTs, MCPs

dv/dt qE/m electric field (in vacuum)

dn/dt primary ionisation, multiplication

v $t \cdot qE / m$ electric field

 

- Vacuum devices
- Electron multiplication
- Low capacitance
- High electric fields

Fast detectors

Sub-nanosecond: 10-100 ps rise-time


Fast

	Signals	Rise-time	Time resolution
Solid state			
• APDs	10^2	300 ps	50 ps
• Silicon PMs	10^7	700 ps	200 ps
• 3D Silicon	10^4	500ps	?

Very fast

• Multi-anode/mesh PMTs	10^7	200ps	50 ps
• MCP PMTs	10^6	150 ps	20-30 ps
• Multi anodes MCP PMTs		30 ps ?	1 ps ?



3D Silicon detectors vs Planar

 

Cinzia Da Via, Brunel, UK 11/2004

Jean-François Genat, Fast Timing Workshop, March 8th 2007, DAPNIA, Saclay

MCP PMT single photon signals

  

Actual MCP PMTs signals
K. Inami et al
Univ. Nagoya
Tr = 500ps
tts= 30ps

MCP PMTs segmented anode signals **simulation**
tts = 860 fs
M. Sanders & H. Frisch,
Univ. Chicago, Argonne

N photo-electrons improves as \sqrt{N}

- Fast detectors, fast signals
- Time pick-off
- Time to Digital conversion
- State of the art
- Technologies
- Conclusion

Fast timing



Electronics gain-bandwidth should match:

- Detector sensitivity
- Detector rise-time

Example: Multi-anodes MCP PMTs:


Rise-time:	25ps
Corresponding Bandwidth:	15 GHz

Effects of amplitude, rise-time

  


Amplitude and/or **Rise-time** spectra translate into **time spread**

Effect of noise

 


Time spread proportional to rise-time

Leading edge

 

Time spread proportional to rise-time


Other effects

 

Walk: Discriminator delay depends on slope across threshold
→ (detector rise-time ⊕ amplifier)
Use appropriate (gain × bandwidth) technology



Zero crossing

 - Use zero-crossing of signal derivative
Detects signal's maximum



Double Threshold

  
- High Threshold to trigger
- Low threshold to time




Avoids noise on low threshold
Decision on very first signal rise

Constant Fraction

 If rise-time proportional to amplitude, use constant-fraction




 If no rise-time dependence with amplitude. Leading edge OK
But detector presumably saturated, and slow down !



If pulse shape independent of amplitude, use Constant fraction

Leading Edge vs CFD

 

Constant Fraction

Three main parameters:

- Trigger threshold
- Delay
- Fraction

Maximize slope at zero-crossing
Carefully optimize wrt signals properties

H. Spieler [IEEE NS 29 June 1982 pp1142-1158]
T.J. Paulus [IEEE NS 32 June 1985 pp 1242-1249]

Leading edge + ADC

- If peak amplitude is measured, leading edge can be compensated off-line

Results compare with CFD technique (IEEE NSS 2006 San Diego)

Pulse sampling

Digitize samples over pedestal and signal

Fast analog sampler + ADC: [E. Delagnes, Saclay, this workshop]

Assuming the signal waveform is known from the detector and electronics properties:

→ Least square fit yields:


- Amplitude
- Time

Iterate with new values until convergence

LSQF: [W.E. Cleland and E.G. Stern. NIM A 338 pp 467-497]

- *All samples contribute to timing estimation*
- *Very robust to noise*

Pulse sampling

 

MATLAB Simulation with Silicon signals

Better compared to CFD by a factor of two depending on noise properties and signal waveform statistics

- MATLAB simulation package (JFG)

System issues

- Drifts due to environmental conditions
- Power supplies drifts and noise
- Cables/fibers instabilities
 - Cable has shorter group delay, and even higher bandwidth, **may pick-up noise**
 - Micro-coax makes a come-back

Outline

- Fast detectors, Fast signals
- Time pick-off
- Time to Digital conversion
- State of the art
- Technologies
- Conclusion


Time to Digital Coding



- “Coarse” (< 1 GHz) time coding use counters
- “Fine” (1-1000ps) time coding uses either
 - Time to Amplitude coding and ADC
 - or Digital delay lines phased locked on clock (DLL)


Both techniques can be differential or not
If short time range only is required, single TAC or DLL OK.

Architecture

 

Fine timing: Time to Amplitude Converter

 - A voltage ramp is triggered on 'Start', stopped on "Stop"
Stop can be a clock edge
- Amplitude is coded with a conventional ADC




Differential TAC

Differential:


Same as above, ramp goes up at rate v_1 , down at rate $v_2 \ll v_1$

 Time is stretched by $\frac{v_1}{v_2}$, measured using a regular counter



Fine timing: Digital Delay Lines

 
- Locked ring oscillator
Loop of voltage controlled delay elements locked on a clock.
- Generation of subsequent logic transitions distant by τ .
 τ can be as small as 10-100 ps



Total delay $N \tau$ is in the range of half a clock period

Digital Delay Lines: DLL

Delay locked loop

 


Clock feeds the digital delay line
Phase arbiter locks delays on clock period


[M. Bazes IEEE JSSC 20 p 75]

Phase noise

 Due to any analog noise source in the oscillator (thermal, 1/f...)




Power Spectrum:

 

$$j = \frac{f}{2\pi f_0(\Delta f)} \sqrt{\int_{\Delta f} 10^{L(f)/10} df}$$

Atomic Clock Chip

 

Courtesy: NIST


A few mm³

The 'physics package' of the chip-scale atomic clock includes (from the bottom) a laser, a lens, an optical attenuator to reduce the laser power, a waveplate that changes the polarization of the light, a cell containing a vapor of cesium atoms, and (on top) a photodiode to detect the laser light transmitted through the cell. The tiny gold wires provide electrical connections to the electronics for the clock.


Stability

Short time stability: $< 1s$
Long term: $> 1s$

Hydrogen: 1fs/s

 

Phase lock

 


Feedback can be analog (RC filter) or digital using the TDC digital response itself

Delay elements

Active RC element: R resistance of a switched on transistor
C total capacitance at the connecting node

 Typically RC = 1-100 using current IC technologies





$$\sigma_N = \sigma \sqrt{N}$$

σ is technology dependent: the fastest, the best !

Within a chip $\sigma \sim 1\%$
a wafer $\sigma \sim 5-10\%$
a lot $\sigma \sim 10-20\%$

[Mantyniemi et al. IEEE JSSC 28-8 pp 887-894]

  
Time controlled delay element: Starved CMOS inverter



CMOS Technology 90nm: $\tau > \sim 20$ ps
45nm < L < 250nm : 65 nm in production today

Time arbitration

 
SR flip-flop in the "forbidden" state (8 transistors)



Final state depends upon first input activated:



R prior S: $\overline{Q}=1$, $Q=0$

R after S: $\overline{Q}=0$, $Q=1$

 

Issue: metastable states if S and R "almost" synchronous

Time arbitration

  

Six transistors implementation in CMOS


Same metastability issues

[V. Gutnik et al. MIT IEEE 2000 Symp. on VLSI Circuits]

Differential Delay Lines Time Vernier

Fast Stop, catches slow Start

 Time quantum $t_1 - t_2$ as small as technology spreads allow



$$N_{bit} = \frac{1}{2} \log_2(T / \sigma)$$

N_{bit} = number of bits for $\frac{1}{2}$ LSB precision

T = full-scale (maximum time interval to be measured)

σ = delay elements spread

Differential Delay Lines Time Vernier

Work for DELPHI (LEP) Outer Detector (1984):

500 ps binning, 150ps resolution TDC using digital delay lines
2 μm Gate Array technology

This work scaled today : $150 \text{ ps} \times 65\text{nm} / 2000\text{nm} = 4.8 \text{ ps}$


Digital delay lines:

Very short coding delay (no stretch, no ADC delay)

Multipulse Time Vernier

- Multipulse version:
- Generate vernier references at any time
 - Arbiter with incoming start and stops

Clock propagated

 

J. Christiansen (CERN)

Outline

- Fast signals
- Time pick-off
- Time to Digital conversion
- State of the art
- Technologies
- Conclusion

Picosecond chips

Digital

- Vernier delay lines offer 5-100 ps resolution for multi-channel chips

Full custom: 25ps J. Christiansen, CERN

8ps J. Jansson, A. Mantyniemi, J Kostamovaara, Olou Univ Finland

Analog

- 10ps TAC chip available from ACAM (2 channels) if channel rate < 500 kHz, 40ps @40 MHz
- Analog full-custom chips: Argonne is designing disc + TAC full-custom chips for 1 ps in SiGe 250nm HBT technology [F. Tang, this workshop]

Picosecond electronics

- Picosecond resolution hardware

The TCSPC Power Package SPC-134

Four-Channel Time-Correlated Single Photon Counting Module

Four Fully Parallel TCSPC Channels
Ultra-High Data Throughput
Overall Saturated Count Rate 40 MHz
Channel Saturated Count Rate 10 MHz (Dead Time 100ns)
Dual Memory Architecture: Readout during Measurement
Reversed Start/Stop: Repetition Rates up to 200 MHz
Electrical Time Resolution down to 8 ps FWHM / 5 ps rms
Channel Resolution down to 813 fs
Up to 4096 Time Channels / Curve
Measurement Times down to 0.1 ms
Instrument Software for Windows 2000 / NT / XP
Direct Interfacing to most Detector Types
Single Decay Curve Mode
Oscilloscope Mode
Sequential Recording Mode
Spectrum Scan Mode with 8 Independent Time Windows
Continuous Flow Mode
FIFO / Time Tag Mode for FCS, FIDA, FILDA, BIFL

**Becker & Hickl
Germany**

5ps rms @ 200 MHz

Some Costs


■	Becker & Hickl	SPC 134	4-channel 1ps	CFD +TDC	system	7 kEuros/ch
■	ACAM	TDC-GPX	2-channel 10-30ps	TDC	chip	80 Euros
■	ORTEC	935	4-Channel 30ps	CFD	NIM	

Outline

- Fast signals
- Time pick-off
- Time to Digital conversion
- State of the art
- Technologies
- Conclusion

CMOS Technologies

CMOS

 


CMOS from 90 to 45 nm technology nodes (ITRS 2005)

Technologies

SiGe HBTs 220 GHz MPW from IHP IBM

 - Ned Spencer (UCSC) LHC [Perugia FEE 2006]
- Fukun Tang (Univ Chicago) Picosecond timing [this workshop]




ITRS from 2003 to 2008 (2005)

Outline

- Fast signals
- Time pick-off
- Time to Digital conversion
- State of the art
- Technologies
- Conclusion

3D imaging using fast Timing with APDs array

 - C. Niclass et al. [EPF Lausanne, Switzerland, 2006]
 - Close to SiPM devices (Geiger mode, self-quenching by pulse current avalanche through MOS transistor)
 - On chip readout electronics
- tts from APDs < 50 ps
- Overall 300 ps resolution (TDC dominated) resulting in a 1.8mm spatial resolution using 10^2 to 10^4 points



Human face depth map and profile (in mm)

**Today, 10 ps is integrated
1 ps under work, looks promising from very fast VLSI technologies**

The End